



ARRL Periodicals Archive – Search Results

A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.


For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Dec 1968

Title: Combine VHF Bandpass Filters

Author: Reed E. Fisher, W2CQH

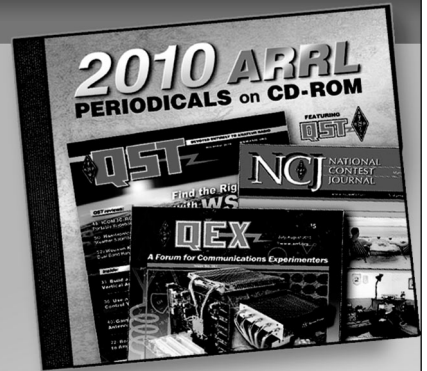[Click Here to Report a Problem with this File](#)



2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2010 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at www.adobe.com.

2010 ARRL Periodicals on CD-ROM

ARRL Order No. 2001

Only \$24.95*

*plus shipping and handling

Additional sets available:


2009 Ed., ARRL Order No. 1486, \$24.95
 2008 Ed., ARRL Order No. 9406, \$24.95
 2007 Ed., ARRL Order No. 1204, \$19.95
 2006 Ed., ARRL Order No. 9841, \$19.95
 2005 Ed., ARRL Order No. 9574, \$19.95
 2004 Ed., ARRL Order No. 9396, \$19.95
 2003 Ed., ARRL Order No. 9124, \$19.95
 2002 Ed., ARRL Order No. 8802, \$19.95
 2001 Ed., ARRL Order No. 8632, \$19.95



ARRL The national association for AMATEUR RADIO™

SHOP DIRECT or call for a dealer near you.
 ONLINE WWW.ARRL.ORG/SHOP
 ORDER TOLL-FREE 888/277-5289 (US)

Comblines V.H.F. Bandpass Filters

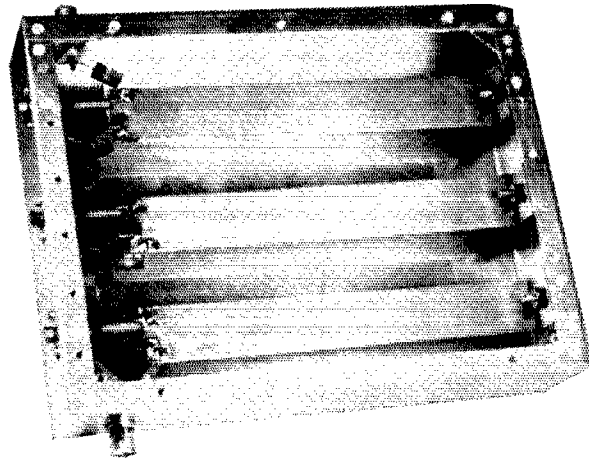

BY REED E. FISHER,* W2CQH

Interior of the 50-MHz. combline filter.

In a previous article¹ it was shown how low-loss multiple-section interdigital bandpass filters could be constructed for 432 and 1296 MHz. These filters are very practical at u.h.f., but when scaled up in size to work on 50 or 144 MHz. they become unwieldy. Interdigital filter theory requires that all the resonators must remain physically a quarter-wave long. Therefore, to reduce the size of v.h.f. filters it is desirable to shorten the resonator lengths by capacitive loading. Cristal² has recently shown how this is accomplished in a straightforward manner that yields a combline structure which is exceedingly simple to build, using stripline techniques. The shortened filter is called "comblines" because, in contrast to the interdigital structure, all resonators are grounded at the same end of the cavity, simulating teeth of a comb. Although Tilton³ has already written an excellent article describing the construction and use of stripline and coaxial filters, they are single-section types that do not yield the passband flatness and out-of-band rejection obtainable with multiple-section structures.

Construction details of three-section combline filters centered near 52, 146 and 222 MHz.


* Forum Court, Morris Plains, N. J. 07950.

¹ R. E. Fisher, "Interdigital Bandpass Filters for Amateur V.H.F./U.H.F. Applications," March, 1968, *QST*, p. 32.

² E. G. Cristal, "Capacity Coupling Shortens Combline Filters," *Microwaves*, Dec. 1967, p. 44.

³ E. P. Tilton, "Coaxial-Tank V.H.F. Filters," *QST*, Oct. 1964, p. 11.

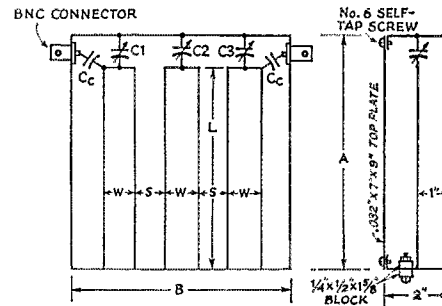
are given in Fig. 1. Each filter is built in a



DIMENSION	52 MHz.	146 MHz.	222 MHz.
A	9"	7"	7"
B	7"	9"	9"
L	7 ³ / ₈ "	6"	6"
S	1"	1 ¹ / ₁₆ "	1 ³ / ₁₆ "
W	1"	1 ⁵ / ₈ "	1 ⁵ / ₈ "
CAPACITANCE (pf)			
C1	110	22	12
C2	135	30	15
C3	110	22	12
C _c	35	6.5	2.8

Fig. 1—Schematic diagram and principal structural details for combline v.h.f. filters.

Fig. 2—Bandpass characteristics of the 50-MHz. combline filter, compared with those of a single-section filter.

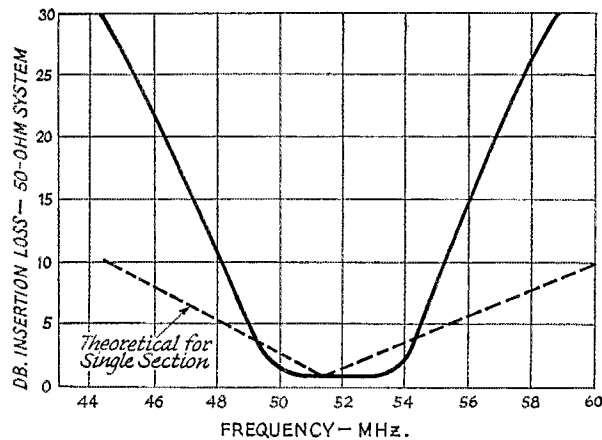

standard 7 x 9 x 2-inch aluminum chassis (Bud AC-406). The three resonators are made of 0.032-inch flashing copper and spaced one inch from the chassis bottom. Each resonator is firmly clamped to a chassis sidewall by two $\frac{1}{4}$ x $\frac{1}{2}$ x $1\frac{3}{8}$ -inch brass blocks. Alternate clamping methods may be tried, but the joints must be secure since large r.f. currents flow in this region, and the best possible electrical connection is mandatory. The tuning capacitors C_1 , C_2 , and C_3 are APC air trimmers, paralleled, when necessary, with mica capacitors. The coupling capacitors, C_c , are fixed micas or ceramic trimmers. Note that there are no coupling capacitors between resonators; the necessary coupling is obtained by the electromagnetic fields within the cavity. If the filters are to pass more than about ten watts the mica capacitors should be replaced by equivalent air units having adequate plate spacing.

An aluminum cover, 7 x 9 by 0.032 inches in size, which serves as the top groundplane, is fastened over the chassis opening with No. 6 sheet metal screws. At least six screws should be used in the groundplane edges that face the resonator ends.

The filter can be aligned roughly by individually grid-dipping each resonator with the top cover removed, and with 50-ohm loads attached to each BNC connector. A temporary partial top groundplane, at least double the resonator width, must be clamped over the resonator being dipped, since the cover affects the resonant frequency. Alignment is completed by installing the filter in the system and adjusting all tuning capacitors until maximum signal transmission is obtained at the desired center frequency.

The measured characteristics of the 50-MHz. filter in a 50-ohm system are given in Fig. 2. The filter has a "maximally-flat" response. The 3-dB bandwidth is about 5 MHz., and the midband (52 MHz.) insertion loss is 0.6 dB. The dotted curve is the theoretical response of a single-section coaxial or stripline filter having the same 3-dB bandwidth. It is evident that the three-section filter gives steeper out-of-band rejection, yet does not have to be retuned when the frequency is moved across the band.

The two-meter filter's measured characteristics are shown in Fig. 3. The 3-dB bandwidth was again about 5 MHz., and the midband (146 MHz.) insertion loss was 0.7 dB. The 220-MHz. filter was not constructed but should give a 6-MHz. 3-dB bandwidth and low midband loss.

If the filters are to be used in a 75-ohm system, the coupling capacitor value should be multiplied by $\sqrt{50/75}=0.82$. For example, the new value of coupling capacitors in the six-meter filter would be $0.082 \times 36 \text{ pf.} = 30 \text{ pf.}$ All other capacitors and dimensions should remain unchanged.

Hopefully these structures should solve the most knotty v.h.f. filtering problem. QST

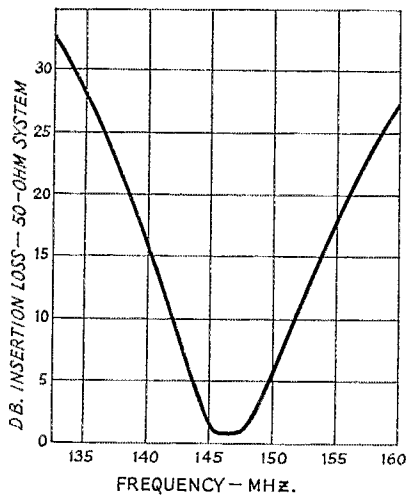


Fig. 3—Characteristics of the 144-MHz. filter.